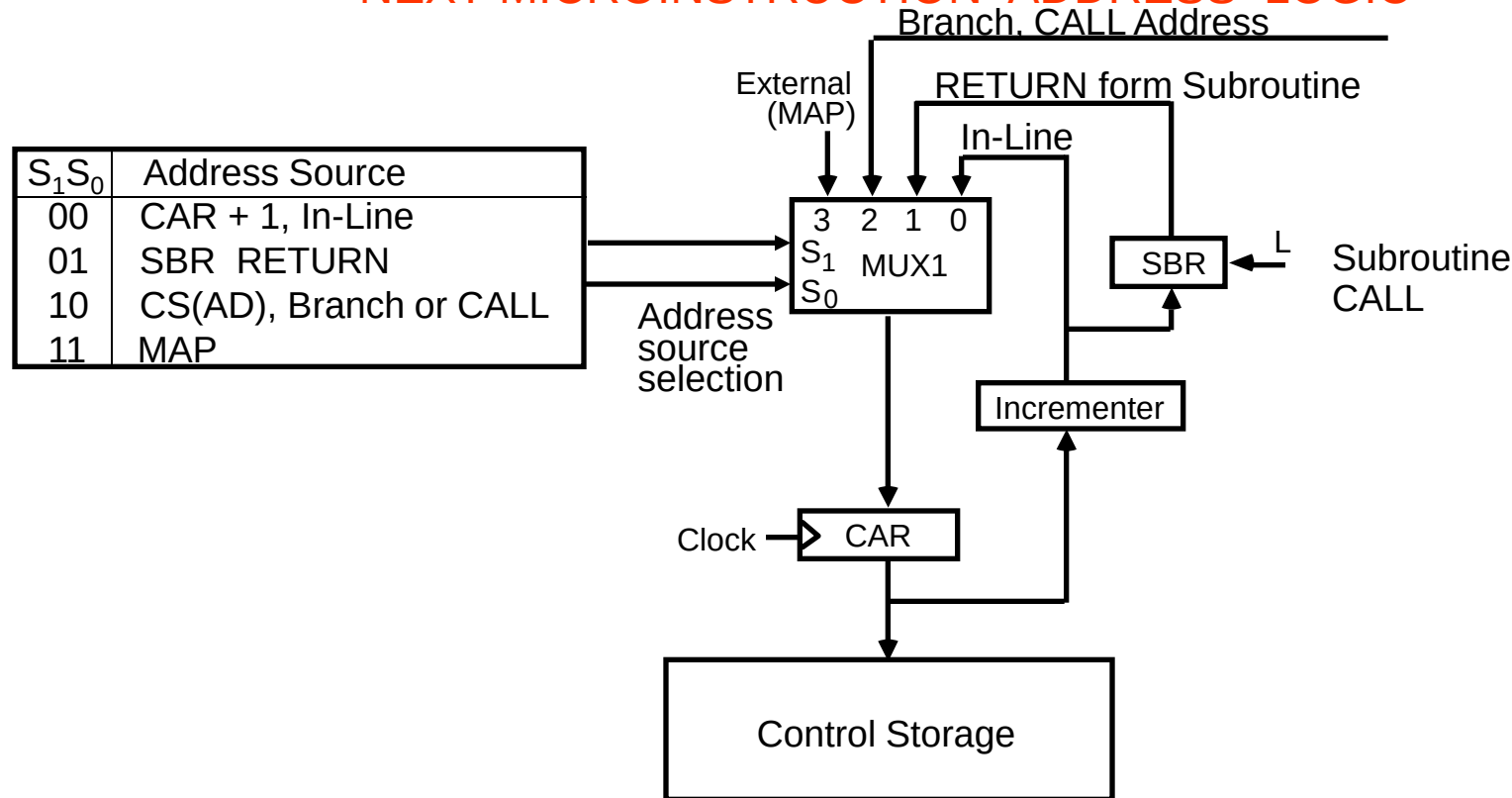


MICROPROGRAM SEQUENCER

- NEXT MICROINSTRUCTION ADDRESS LOGIC -




MUX-1 selects an address from one of four sources and routes it into a CAR

- In-Line Sequencing $\rightarrow$ CAR + 1
- Branch, Subroutine Call $\rightarrow$ CS(AD)
- Return from Subroutine $\rightarrow$ Output of SBR
- New Machine instruction $\rightarrow$ MAP



MICROPROGRAM SEQUENCER

- CONDITION AND BRANCH CONTROL -

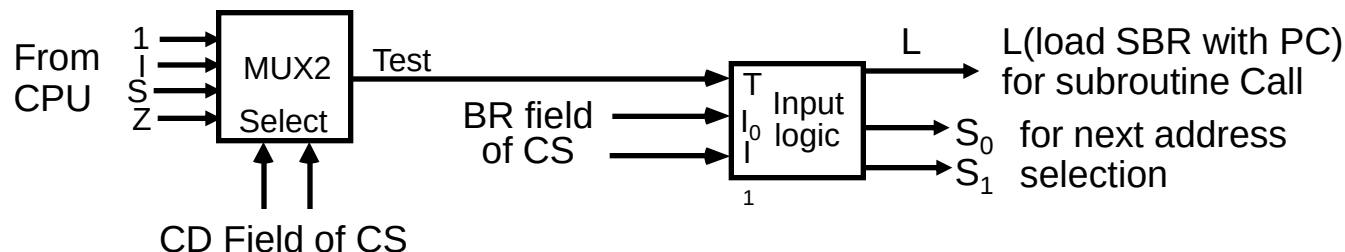

Input Logic

$I_1 I_0 T$	Meaning	Source of Address	$S_1 S_0$	L
000	In-Line	CAR+1	00	0
001	JMP	CS(AD)	01	0
010	In-Line	CAR+1	00	0
011	CALL	CS(AD) and SBR <- CAR+1	01	1
10x	RET	SBR	10	0
11x	MAP	DR(11-14)	11	0

$$\begin{aligned}
 S_1 &= I_1 \\
 S_0 &= I_1 I_0 + I_1' T \\
 L &= I_1' I_0 T
 \end{aligned}$$



MICROPROGRAM SEQUENCER

