

REGISTER TRANSFER LANGUAGE

- Rather than specifying a digital system in words, a specific notation is used, *register transfer language*
- For any function of the computer, the register transfer language can be used to describe the (sequence of) microoperations
- Register transfer language
 - A symbolic language
 - A convenient tool for describing the internal organization of digital computers
 - Can also be used to facilitate the design process of digital systems.



DESIGNATION OF REGISTERS

- Registers are designated by capital letters, sometimes followed by numbers (e.g., **A**, **R13**, **IR**)
- Often the names indicate function:
 - MAR - memory address register
 - PC - program counter
 - IR - instruction register
- Registers and their contents can be viewed and represented in *various ways*
 - A register can be viewed as a single entity:





- Registers may also be represented showing the bits of data they contain



DESIGNATION OF REGISTERS

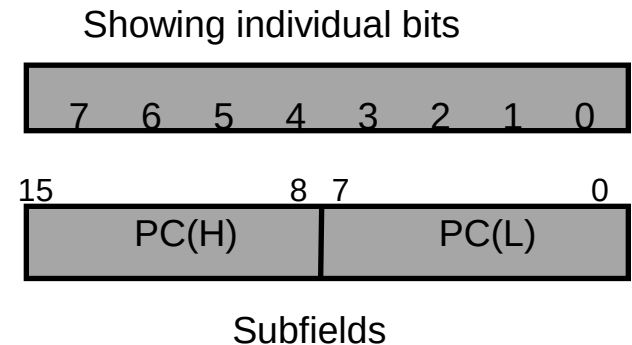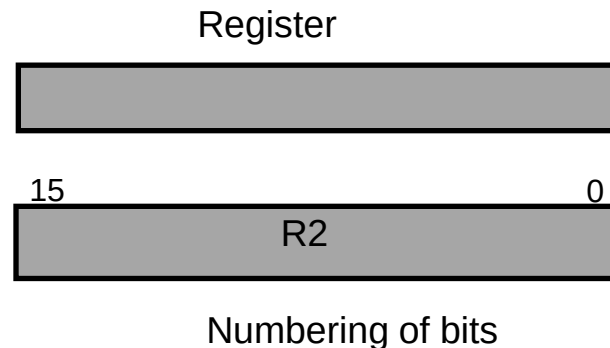- Designation of a register
 - a register
 - portion of a register
 - a bit of a register
- Common ways of drawing the block diagram of a register



REGISTER TRANSFER

- Copying the contents of one register to another is a register transfer
- A register transfer is indicated as

$$R2 \leftarrow R1$$

- In this case the contents of register R1 are copied (loaded) into register R2
- A simultaneous transfer of all bits from the source R1 to the destination register R2, during one clock pulse
- Note that this is a non-destructive; i.e. the contents of R1 are not altered by copying (loading) them to R2



REGISTER TRANSFER

- A register transfer such as

$R3 \leftarrow R5$

Implies that the digital system has

- the data lines from the source register (R5) to the destination register (R3)
- Parallel load in the destination register (R3)
- Control lines to perform the action



CONTROL FUNCTIONS

- Often actions need to only occur if a certain condition is true
- This is similar to an “if” statement in a programming language
- In digital systems, this is often done via a *control signal*, called a *control function*
 - If the signal is 1, the action takes place
- This is represented as:

$P: R2 \leftarrow R1$

Which means “if $P = 1$, then load the contents of register R1 into register R2”, i.e., if $(P = 1)$ then $(R2 \leftarrow R1)$




HARDWARE IMPLEMENTATION OF CONTROLLED TRANSFERS


- Implementation of controlled transfer

P: $R2 \leftarrow R1$

Block diagram

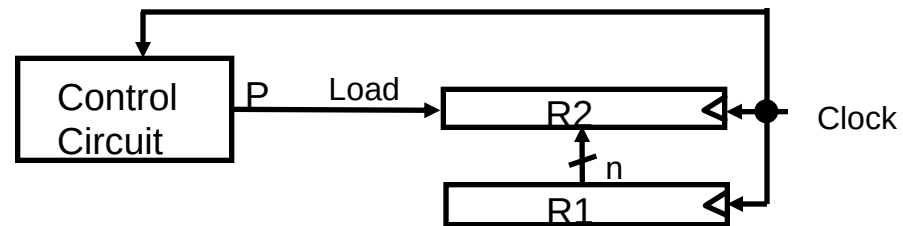

Timing diagram

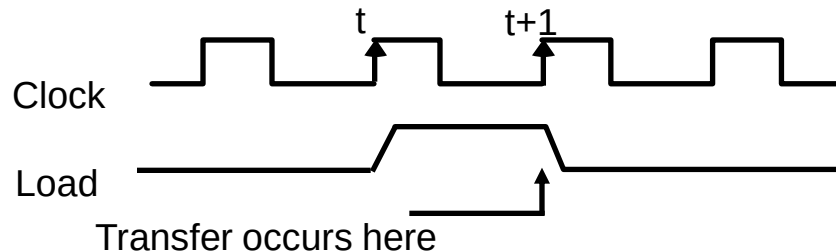

- The same clock controls the circuits that generate the control function and the destination register
- Registers are assumed to use *positive-edge-triggered* flip-flops



SIMULTANEOUS OPERATIONS

- If two or more operations are to occur simultaneously, they are separated with commas
 - P: $R3 \leftarrow R5, MAR \leftarrow IR$
- Here, if the control function $P = 1$, load the contents of R5 into R3, and at the same time (clock), load the contents of register IR into register MAR

